

SARDAR PATEL UNIVERSITY
BSc (IV Sem.) Examination
Wednesday, 10th April 2013
11 am - 2 pm

US04CELE01 – Electronics Devices and Applications

Total Marks: 70

Note: Figures to the right indicate full marks.

Q.1 Multiple Choice Questions: [10]

- (1) In a frequency response curve the output normally remains constant over the _____ range of frequencies.
 (i) high (ii) low (iii) middle
- (2) Decibel is a unit of _____ change.
 (i) Voltage (ii) Current (iii) Power
- (3) The _____ is sometimes called anipolar transistor.
 (i) BJT (ii) FET (iii) UJT
- (4) In an enhancement mode MOSFET The conductivity of the channel is enhanced by the positive bias on the _____.
 (i) drain (ii) gate (iii) source
- (5) _____ is the best FET biasing circuit.
 (i) self bias (ii) potential divider bias (iii) fixed voltage bias
- (6) In enhancement depletion mOSFET drain current is _____ when $v_{gs}=0$.
 (i) absent (ii) present (iii) non-continuous
- (7) The common source circuit is also called _____ circuit.
 (i) source follower (ii) grounded source (iii) grounded drain
- (8) The dynodes are electrodes which are treated to produce _____.
 (i) primary (ii) secondary (iii) neutron
- (9) In common source circuit the input and output signals are _____ phase with each other.
 (i) 90° out of (ii) 180° out of (iii) 270° out of
- (10) The cadmium sulfide photoconductive cell responds to _____ light.
 (i) ultraviolet (ii) visible (iii) infrared

Q.2 Answer any ten questions in brief. [20]

- (1) Define bias point.
- (2) Why does the amplifier gain falls at low frequencies?
- (3) Give the constructional details of n-channel JFET.
- (4) Define decibels.
- (5) Draw the common source ac equivalent circuit.
- (6) Draw the self bias circuit using n-channel JFET.
- (7) Draw the potential divider circuit using p-channel JFET.
- (8) Why common drain circuit is called source follower?
- (9) Draw the common drain ad equivalent circuit.
- (10) What is an LED?
- (11) State the used of photoconductive cell.
- (12) What is dynamic scattering?

- Q.3
(a) Explain the frequency response curve of an amplifier. [06]
(b) Explain the drain characteristics of an n-channel JFET with an external bias. [04]

OR

- Q.3
(a) Discuss in detail the drain characteristics of n-channel JFET when $V_{GS}=0$. [05]
(b) Discuss in detail the depletion regions of n-channel JFET. [05]

- Q.4
(a) Discuss in detail the enhancement mode MOSFET. [06]
(b) Explain the self bias circuit of FET. [04]

OR

- Q.4
(a) Discuss in detail the depletion enhancement mode MOSFET. [06]
(b) Draw the potential divides bias circuit for a FET and explain its working. [04]

- Q.5
(a) Draw the circuit of common Gate Amplifier and explain its working. [06]
(b) Draw the circuit of common Drain Amplifier and explain its working. [04]

OR

- Q.5 Draw the circuit of common Source Amplifier and explain its working. [10]

- Q.6
(a) Discuss in detail the Photomultiplier Tube. [07]
(b) Write a note on Optoelectronic Coupler. [03]

OR

- Q.6
(a) Discuss in detail the Photoconductive Cell. [06]
(b) Write a note on Solar Cell. [04]

*** * ***